

**AG-1134**

B.Sc. (Part - I)

Term End Examination, 2018-19

COMPUTER SCIENCE

Paper - I

Time : Three Hours]

[Maximum Marks : 50

Note : Answer **all** questions. The figures in the right-hand margin indicate marks. Answer should be brief and to the point. Draw diagrams to justify your answers. Assume suitable data if required.

Unit-I

1. (a) What are the different types of software ?
Explain. 5

(b) Draw and discuss the block diagram of
CPU. 5

OR

(a) Write about the following : 5

(i) Monitor

(ii) Mouse

(2)

(b) Convert the following : 5

(i) $8FE2 = ()_{10}$

(ii) $(1011001) = ()_{10}$

Unit-II

2. (a) Discuss the basic logic gates with truth table. 5

(b) Explain positive logic and negative logic with suitable example. 5

OR

(a) Discuss the following : 5

(i) Binary Code

(ii) Gray Code

(b) Why digital circuits can be represented by Boolean equations ? Explain your answer. 5

Unit-III

3. (a) Explain the following : 5

(i) Propagation delay

(ii) DeMorgan's theorem

(b) Draw and discuss the half adder and full adder. 5

OR**430_BSP_(3)****(Continued)**

(3)

Simplify the following expression using
K-map. 10

$$f(w, x, y, z) = x'yz + wxz + w'x'yz + yz'$$

Unit-IV

4. (a) Draw and discuss the, 4-bit binary parallel adder. 5
(b) Discuss the concept of Edge triggered flip-flop with suitable example. 5

OR

(a) Draw and discuss multiplexer in detail. 5
(b) Explain bistable circuits and write its advantages. 5

Unit-V

5. (a) Write the applications of shift registers. 5
(b) Draw and discuss down counter. 5

OR

(a) Explain the following : 5
 (i) EPROM
 (ii) ROM
(b) Discuss the concept of code-7 precision time interval. 5
