

PD – 371 CV-19
(523) M.Sc. PHYSICS (Third SEM.)
Term End Examination DEC. 2020
ELECTRONICS - III

Time : Three Hours]

[Maximum Marks : 080]

[Minimum Pass Marks :

नोट:- दोनों खण्डों से निर्देशानुसार उत्तर दीजिए। प्रश्नों के अंक उनके दाहिनी ओर अंकित हैं।

Note: Answer From Both the Section as Directed. The Figures in the right-hand margin indicate marks.

खण्ड /SECTION-A

1. Answer the following questions. 1x10

- (a) flip -flop is.....device.
- (b) R- 2R ladder network method isconverter.
- (c) fullform of IC is
- (d) 1's complement of 1010 is
- (e) Add $1011 + 1001 =$
- (f) BCD code of 27 is
- (g) 1 line to 16line converter is called.....
- (h) Convert the binary number 0.011 to its decimal equivalent.
- (i) Convert the hexadecimal number CA to its decimal number.
- (j) full form of CMOS,.....

2. Answer the following questions. 2x5

- (a) Write De-Morgan's theorem statement.
- (b) Define Ex-NOR Gate.
- (c) Draw 1's complement subtracter circuit.
- (d) Draw The circuit diagram of JK Master slave flip-flop.
- (e) Write difference between A/D and D/A converter.

खण्ड /SECTION-B

1. Answer all question:-

UNIT-I

3.(a) Define Decimal, Binary, Octal and Hexadecimal number system. 7
 (b) Explain BCD code, Excess-3 code, gray code? 8

OR

(a) Define all logic Gate (OR Gate) AND Gate Not Gate, NAND Gate, NOR Gate) 7
 (b) What is K-map? Explain K-map for four variable. 8

UNIT-II

4.(a) Explain Half adder and Full adder with circuit diagram and it's truth table. 7
 (b) Define RTL, DTL, TTL, ECL. 8

OR

(a) Define multiplexer and demultiplexer. 7
 (b) Explain BCD to decimal and BCD to seven segment decoder. 8

UNIT-III

5.(a) Explain R-S flip-flop using NOR Gate and NAND Gate with working. 7
 (b) Explain up counter and down counter with working and circuit diagram. 8

OR

(a) Explain Ring counter with time diagram. 7
 (b) Define PIPO, SIPO, PISO, SCSI. 8

UNIT-IV

6.(a) Explain D/A converters using binary weighted resistor network method. 7
 (b) Define A/D converter and explain dual slope converter method. 8

OR

(a) Explain IC technology with its advantages and disadvantages. 7
 (b) Explain basic processes used in monolithic technology. 8